

What is the Boolean expression F represented by the logic circuit diagram below?

a) $F = X \square Y$

b) $F = X + Y$

c) $F = (\neg X \square Y) + (X \square \neg Y)$

d) $F = (\neg X \square \neg Y) + (X \square Y)$